

```

1  /*
2  multiplier_32b is a 32-bit multiplier leveraging both optimization structures: bit-pair
3  recoding and carry-save addition.
4  It accepts M and Q as the multiplication and multiplier, respectively.
5  */
6
7  module multiplier_32b (
8      input [31:0] M, Q,
9      output [63:0] result
10 );
11
12 // All relevant variations of M for booth augend selection.
13 wire [32:0] Q_shifted = {Q, 1'b0}; // Left shifted Q by 1 such that the i-1 Booth check
14 is valid with i = 0.
15 wire [31:0] negM = -M;
16 wire [32:0] Mx2 = {M, 1'b0};
17 wire [32:0] negMx2 = {negM, 1'b0};
18
19 // Augends.
20 reg [63:0] partial_products [15:0];
21
22 integer i;
23 // Perform Booth Augend Selection
24 always @(*) begin
25     for (i = 0; i < 31; i = i+2) begin
26         // Choose variant of M based on partial_products
27         case ({Q_shifted[i+2], Q_shifted[i+1], Q_shifted[i]})
28             // All values are properly sign-extended.
29             3'b000: partial_products[i>>1] = 64'b0; // 0 x M
30             3'b001: partial_products[i>>1] = {{32{M[31]}}, M}; // +1 x M
31             3'b010: partial_products[i>>1] = {{32{M[31]}}, M}; // +1 x M
32             3'b011: partial_products[i>>1] = {{31{Mx2[32]}}, Mx2}; // +2 x M
33             3'b100: partial_products[i>>1] = {{31{negMx2[32]}}, negMx2}; // -2 x M
34             3'b101: partial_products[i>>1] = {{32{negM[31]}}, negM}; // -1 x M
35             3'b110: partial_products[i>>1] = {{32{negM[31]}}, negM}; // -1 x M
36             3'b111: partial_products[i>>1] = 64'b0; // 0 x M
37             default: partial_products[i>>1] = 64'b0;
38         endcase
39         // Apply appropriate shift before addition.
40         partial_products[i>>1] = partial_products[i>>1] << i;
41     end
42 end
43
44 // Final operands after reduction process
45 wire [63:0] reduced1, reduced2;
46
47 // 16-to-2 CSA reducer.
48 CSA_tree_16to2 reduction (.augends(partial_products), .reduced1(reduced1), .reduced2(
49 reduced2));
50
51 // Final carry-propagate stage, with no carry-in, nor carry-out (result for 32-bit mult.
52 is 64-bits)
53 adder_64b carry_propagate (.cin(1'b0), .x(reduced1), .y(reduced2), .s(result)); // No
54 cout.
55
56 endmodule
57
58 `timescale 1ns / 1ps
59
60 module multiplier_32b_tb;
61     reg [31:0] M, Q;
62     wire [63:0] result;
63
64     // Instantiate the multiplier
65     multiplier_32b dut (M, Q, result);
66
67     // Test procedure
68     initial begin
69         // Test cases
70         M = 32'd0; Q = 32'd0; #10; // 0 * 0
71         $display("M=%d, Q=%d, result=%d", M, Q, result);
72     end
73 endmodule

```

```
70
71 M = 32'd15; Q = 32'd10; #10; // 15 * 10
72 $display("M=%d, Q=%d, result=%d", M, Q, result);
73
74 M = -32'd15; Q = 32'd10; #10; // -15 * 10
75 $display("M=%d, Q=%d, result=%d", M, Q, result);
76
77 M = 32'd15; Q = -32'd10; #10; // 15 * -10
78 $display("M=%d, Q=%d, result=%d", M, Q, result);
79
80 M = -32'd15; Q = -32'd10; #10; // -15 * -10
81 $display("M=%d, Q=%d, result=%d", M, Q, result);
82
83 M = 32'h7FFFFFFF; Q = 32'h00000001; #10; // Largest positive * 1
84 $display("M=%d, Q=%d, result=%d", M, Q, result);
85
86 M = 32'h80000000; Q = 32'd1; #10; // Smallest negative * 1
87 $display("M=%d, Q=%d, result=%d", M, Q, result);
88
89 M = 32'hFFFFFFFF; Q = 32'hFFFFFFFF; #10; // -1 * -1
90 $display("M=%d, Q=%d, result=%d", M, Q, result);
91
92 $stop;
93     end
94 endmodule
95
96
```